

The SWR is output in Morse code and as voltage between 1V an 5V.

The resistors and diodes serve only as protection against over voltage.

The inputs should be between 0 and 1.1V. Use suitable voltage divider.